
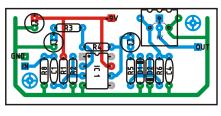


Build the Blue Clipper on this layout. The Blue Clipper didn't have any potentiometers, instead it had an internal trimpot to set the output volume to unity gain. In a new build a regular panel mount potentiometer can be used to be able to use it like a normal volume control. Off board components except for the potentiometers are not shown on the layout. Registered trademarks are property of their owners.

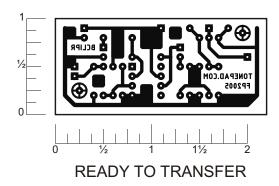

LAYOUT



Γ

ICs

1 - TL071

Resistors	Capacitors	Diodes
R1 - 200k	C1 - 0.047µF	D1 - 1N914
R2 - 240k	C2 - 4.7µF	D2 - 1N914
R3 - 150 ohm	C3 - 4.7µF	
R4 - 150k	C4 - 0.033µF	Other diodes can be used.
R5 - 8k2 (8.2k)	C5 - 100µF	
R6 - 10k `	·	

*Not in original circuit

R7 - 50k trim.

R8 - 2M2 (2.2M)*

All rights reserved. Authorization for personal use only, any commercial use is forbidden.
Permission for posting/serving limited to

##